

PROJECT-10 OUTPUT


Made by: Aashi Srivastava
National Institute of Technology, Warangal

1. A>B

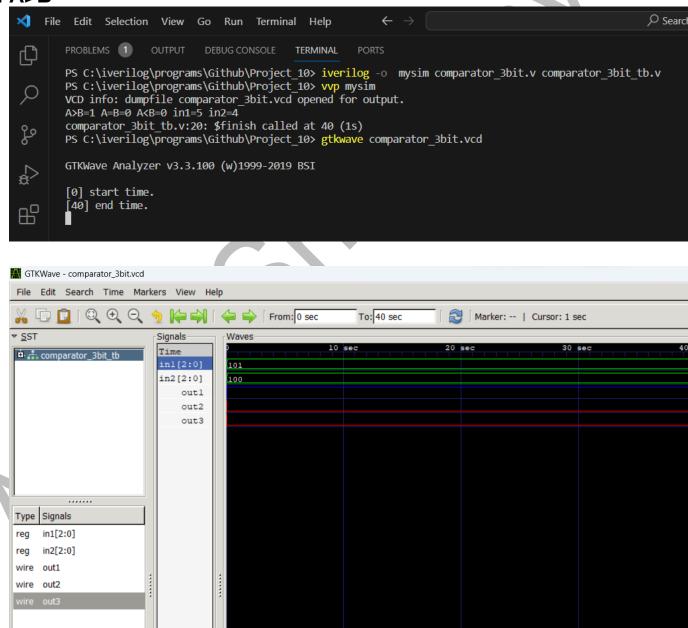

2. A=B

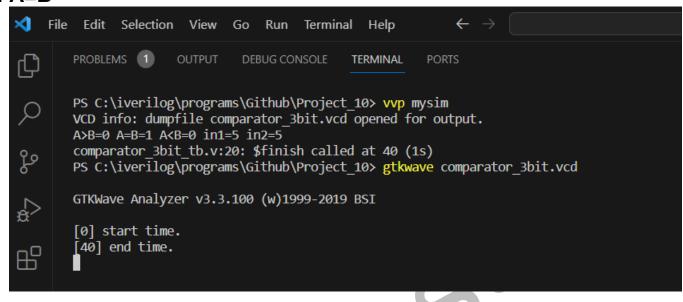

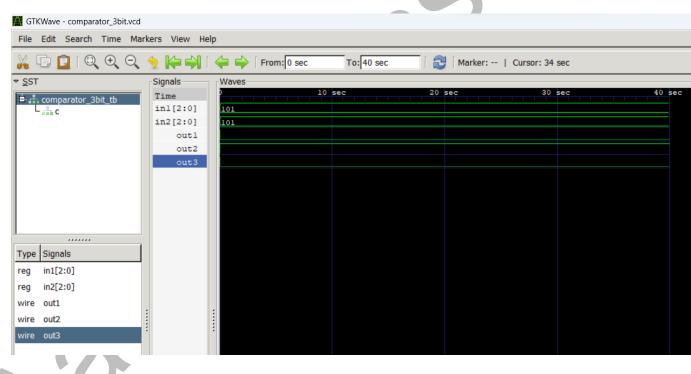

3. A<B

